

Código de Implementación:

Código Completa:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
USE work.paquete.all;

entity contadorUnos is
  Port ( D : in STD_LOGIC_VECTOR (8 downto 0);
        Ini,clr,clk : in STD_LOGIC;
        QA : out STD_LOGIC_VECTOR (8 downto 0);
        dispFin : out STD_LOGIC_VECTOR (6 downto 0));
end contadorUnos;

architecture Behavioral of contadorUnos is

  SIGNAL UC_LA : STD_LOGIC;
  SIGNAL UC_EA : STD_LOGIC;
  SIGNAL UC_Z : STD_LOGIC;
  SIGNAL UC_LB : STD_LOGIC;
  SIGNAL UC_EB : STD_LOGIC;
  SIGNAL UC_EC : STD_LOGIC;
  --**SEÑALES UNIDAD DE CONTROL

  SIGNAL salidaContador : STD_LOGIC_VECTOR(3 downto 0);
  --**SEÑALES CONTADOR

  SIGNAL salidaArreglo : STD_LOGIC_VECTOR(8 downto 0);
  --**SEÑALES ARREGLO

  SIGNAL salidaDecodificador : STD_LOGIC_VECTOR(6 downto 0);
  --**SEÑALES DECODIFICADOR

  SIGNAL reloj : STD_LOGIC;
begin
  UC_z <= not(salidaArreglo(8) or salidaArreglo(7) or salidaArreglo(6) or salidaArreglo(5) or salidaArreglo(4)
or salidaArreglo(3) or salidaArreglo(2) or salidaArreglo(1) or salidaArreglo(0));

  Divisor : divisorFrecuencia
    Port map(
      clr => clr,
      clk => clk,
      frecuenciaFin => reloj
    );
  --**DIVISOR DE FRECUENCIA

  UC : cartaASM
    Port map(
      Ini => Ini,
      clr => clr,
      clk => reloj,
      LA => UC_LA,
      EA => UC_EA,
```

```

    A0 => salidaArreglo(0),
    Z => UC_Z,
    LB => UC_LB,
    EB => UC_EB,
    EC => UC_EC
);

```

Cont : Contador

```

Port map (
    clk => reloj,
    clr => clr,
    LB => UC_LB,
    EB => UC_EB,
    QB => salidaContador
);

```

Arregl : Arreglo

```

Port map (
    DA => D,
    clk => reloj,
    clr => clr,
    LA => UC_LA,
    EA => UC_EA,
    QA => salidaArreglo
);

```

--**ARREGLO

Decodificado : Decodificador

```

Port map(
    salidaCont => salidaContador,
    display => salidaDecodificador
);

```

--**DECODIFICADOR

mu : mux

```

Port map(
    salidaDeco => salidaDecodificador,
    op => UC_EC,
    salidaMux => dispFin
);

```

--**MUX

QA <= salidaArreglo;

end Behavioral;

Código Divisor:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity divisorFrecuencia is

```

    Port ( clr, clk : in STD_LOGIC;
          frecuenciaFin : out STD_LOGIC);

```

end divisorFrecuencia;

architecture Behavioral of divisorFrecuencia is

```

signal temp : std_logic := '0';
signal conta : integer range 0 to 49999 := 0;
begin
  process(clr,clk) is
  begin
    if(clr = '0')then
      temp <= '0';
      conta <= 0;
    elsif(rising_edge(clk)) then
      if(conta = 49999) then
        temp <= not temp;
        conta <= 0;
      else
        conta <= conta + 1;
      end if;
    end if;
  end process;
  frecuenciaFin <= temp;
end Behavioral;

```

Código UC:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity cartaASM is
  Port ( clk,clr,ini,z,a0 : in STD_LOGIC;
        la,lb,ea,eb,ec : out STD_LOGIC);
end cartaASM;

architecture Behavioral of cartaASM is
  type estados is (e0,e1,e2);
  signal edo_act, edo_sig : estados;
begin

  process(clk,clr)
  begin
    if(clr = '1') then
      edo_act <= e0;
    elsif(rising_edge(clk)) then
      edo_act <= edo_sig;
    end if;
  end process;

  UC : process(edo_act,ini,z,a0)
  begin

    LA <= '0';
    EA <= '0';
    LB <= '0';
    EB <= '0';
    EC <= '0';
    case edo_act is

      when e0 =>

```

```

    LB <= '1';
    if(ini = '1') then
        edo_sig <= e1;
    else
        LA <= '1';
        edo_sig <= e0;
    end if;
when e1 =>
    EA <= '1';
    if(z = '1') then
        edo_sig <= e2;
    elsif(a0 = '1') then
        EB <= '1';
        edo_sig <= e1;
    else
        edo_sig <= e1;
    end if;
when e2 =>
    EC <= '1';
    if(ini = '1') then
        edo_sig <= e2;
    else
        edo_sig <= e0;
    end if;
end case;

end process;

end Behavioral;

```

Código Contador:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Contador is
    Port ( LB,EB,clr,clk : in STD_LOGIC;
          QB : inout STD_LOGIC_VECTOR (3 downto 0));
end Contador;

architecture Behavioral of Contador is
    signal DB : STD_LOGIC_VECTOR(3 downto 0);
begin
    DB <= (others => '0');
    process(clk,clr)
    begin
        if(clr = '1') then
            QB <= (others => '0');
        elsif rising_edge(clk) then
            if(LB = '0' and EB = '0') then
                QB <= QB;
            elsif(LB = '1' and EB = '0') then
                QB <= DB;
            elsif(LB = '0' and EB = '1') then

```

```

        QB <= QB + 1;
    end if;
end if;
end process;

```

end Behavioral;

Código Arreglo:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Arreglo is
    Port ( DA : in STD_LOGIC_VECTOR (8 downto 0);
          la,ea,clk,clr : in STD_LOGIC;
          QA : inout STD_LOGIC_VECTOR (8 downto 0));
end Arreglo;

```

architecture Behavioral of Arreglo is

```

begin
process ( clr,clk)
begin
    if( clr = '1') then
        QA <= (others => '0');
    elsif rising_edge(clk) then
        if(LA = '0' and EA = '0') then
            QA <= QA;
        elsif(LA = '1' and EA = '0') then
            QA <= DA;
        elsif(LA = '0' and EA = '1')then
            for i in 0 to 7 loop
                QA(i)<=QA(i+1);
            end loop;
            QA(8)<='0';
        end if;
    end if;
end process;

```

end Behavioral;

Código MUX:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux is
    Port ( salidaDeco : in STD_LOGIC_VECTOR (6 downto 0);
          op : in STD_LOGIC;
          salidaMux : out STD_LOGIC_VECTOR (6 downto 0));
end mux;

```

architecture Behavioral of mux is

```

constant def : STD_LOGIC_VECTOR(6 DOWNT0 0) := "1111110";
begin
    salidaMux <= salidaDeco when op = '1' else def;
end Behavioral;

```

Códigos de simulación:

Código Completa:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity TB_UC is
-- Port ( );
end TB_UC;

architecture Behavioral of TB_UC is

component contadorUnos is
  Port ( D : in STD_LOGIC_VECTOR (8 downto 0);
        Ini,clr,clk : in STD_LOGIC;
        QA : out STD_LOGIC_VECTOR (8 downto 0);
        dispFin : out STD_LOGIC_VECTOR (6 downto 0));
end component;
SIGNAL D : STD_LOGIC_VECTOR (8 downto 0);
SIGNAL Ini,clr,clk : STD_LOGIC;
SIGNAL QA : STD_LOGIC_VECTOR (8 downto 0);
SIGNAL dispFin : STD_LOGIC_VECTOR (6 downto 0);
constant CLK_period : time := 10 ns;
begin

u1 : contadorUnos
  Port map(
    D => D,
    ini => ini,
    clr => clr,
    clk => clk,
    QA => QA,
    dispFin => dispFin
  );

CLK_process :process
begin
  CLK <= '0';
  wait for CLK_period/2;
  CLK <= '1';
  wait for CLK_period/2;
end process;

entradas: process
begin
  clr<='1';
  d<="101101011";
  ini<='0';
  wait for 30 ns;
  clr<='0';
  wait for 30 ns;
  ini<='1';
  wait for 120 ns;

```

```

clr<='1';
d<="000011101";
ini<='0';
wait for 30 ns;
clr<='0';
wait for 30 ns;
ini<='1';
wait for 120 ns;

```

```

clr<='1';
d<="000010000";
ini<='0';
wait for 30 ns;
clr<='0';
wait for 30 ns;
ini<='1';
wait for 120 ns;

```

```

clr<='1';
d<="100001000";
ini<='0';
wait for 30 ns;
clr<='0';
wait for 30 ns;
ini<='1';
wait for 120 ns;

```

```

clr<='1';
d<="000000000";
ini<='0';
wait for 30 ns;
clr<='0';
wait for 30 ns;
ini<='1';
wait for 120 ns;

```

```

wait;
end process;
end Behavioral;

```

Código UC:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity TB_UC_S is
    --PORT
end TB_UC_S;

architecture Behavioral of TB_UC_S is
component cartaASM is

```

```

    Port ( clk,clr,ini,z,a0 : in STD_LOGIC;
           la,lb,ea,eb,ec : out STD_LOGIC);
end component;
SIGNAL clk,clr,ini,z,a0 : STD_LOGIC;
SIGNAL la,lb,ea,eb,ec : STD_LOGIC;
constant clk_period: time := 10 ns;

```

begin

u1 : cartaASM

```

    Port map(
        clk => clk,
        clr => clr,
        ini => ini,
        z => z,
        a0 => a0,
        la => la,
        lb => lb,
        ea => ea,
        eb => eb,
        ec => ec
    );

```

CLK_process :process

begin

CLK <= '0';

wait for CLK_period/2;

CLK <= '1';

wait for CLK_period/2;

end process;

stimulus: process

begin

ini<='0';

a0<='0';

z<='0';

clr<='1';

wait for 30 ns;

clr<='0';

wait for 60 ns;

ini<='1';

wait for 10 ns;

ini<='0';

wait for 50 ns;

a0<='1';

wait for 10 ns;

a0<='0';

wait for 20 ns;

a0<='1';

wait for 10 ns;

a0<='0';

wait for 120 ns;

z<='1';

wait;

end process;

end Behavioral;

Código Arreglo:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity TB_Arreglo is
-- Port ( );
end TB_Arreglo;

architecture Behavioral of TB_Arreglo is
component Arreglo is
    Port ( DA : in STD_LOGIC_VECTOR (8 downto 0);
          la,ea,clk,clr : in STD_LOGIC;
          QA : inout STD_LOGIC_VECTOR (8 downto 0));
end component;

SIGNAL DA : STD_LOGIC_VECTOR (8 downto 0);
SIGNAL la,ea,clk,clr : STD_LOGIC;
SIGNAL QA : STD_LOGIC_VECTOR (8 downto 0);
constant clk_period: time := 10 ns;
begin
u2 : Arreglo
    Port map(
        DA => DA,
        la => la,
        ea => ea,
        clk => clk,
        clr => clr,
        QA => QA
    );

CLK_process :process
begin
    CLK <= '0';
    wait for CLK_period/2;
    CLK <= '1';
    wait for CLK_period/2;
end process;

stimulus: process
begin
    LA <= '0';
    EA <= '0';
    DA <= "001001110";
    clr<='1';
    wait for 30 ns;
    clr<='0';
    wait for 60 ns;
    LA<='1';
    wait for 50 ns;
    LA <= '0';
    EA <= '1';
    wait for 50 ns;
    DA <= "011101110";
    clr<='1';
    wait for 30 ns;

```

```

clr<='0';
    wait for 60 ns;
LA<='1';
    wait for 50 ns;
LA <='0';
EA <= '1';
    wait for 50 ns;
    wait;
end process;

```

end Behavioral;

Código Contador:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Contador is
-- Port ( );
end TB_Contador;

architecture Behavioral of TB_Contador is
component Contador is
    Port ( LB,EB,clr,clk : in STD_LOGIC;
           QB : inout STD_LOGIC_VECTOR (3 downto 0));
end component;
SIGNAL LB,EB,clr,clk : STD_LOGIC;
SIGNAL QB : STD_LOGIC_VECTOR (3 downto 0);
constant CLK_period : time := 10 ns;
begin
u3 : Contador
    Port map(
        LB => LB,
        EB => EB,
        clr => clr,
        clk => clk,
        QB => QB
    );
CLK_process :process
begin
    CLK <= '0';
    wait for CLK_period/2;
    CLK <= '1';
    wait for CLK_period/2;
end process;

stimulus: process
begin
    clr<='1';
    wait for 30 ns;
    clr<='0';
    wait for 30 ns;
    LB<='0';
    EB<='0';

```

```

wait for 30 ns;
LB<='1';
EB<='0';
wait for 30 ns;
LB<='0';
EB<='1';
wait for 30 ns;
LB<='0';
EB<='1';
wait for 30 ns;
LB<='0';
EB<='1';
wait for 30 ns;
wait;
end process;
end Behavioral;

```

Código Decodificador:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Decodificador is
-- Port ( );
end TB_Decodificador;

architecture Behavioral of TB_Decodificador is
component Decodificador is
    Port ( salidaCont : in STD_LOGIC_VECTOR (3 downto 0);
          display : out STD_LOGIC_VECTOR (6 downto 0));
end component;
SIGNAL salidaCont : STD_LOGIC_VECTOR (3 downto 0) := "0000";
SIGNAL display : STD_LOGIC_VECTOR (6 downto 0) := "0000000";

begin

u4 : Decodificador
    Port map(
        salidaCont => salidaCont,
        display => display
    );

stimulus: process
begin
salidaCont <= "0000";
wait for 30 ns;
salidaCont <= "0001";
wait for 30 ns;
salidaCont <= "0010";
wait for 30 ns;
salidaCont <= "0011";
wait for 30 ns;
salidaCont <= "0100";
wait for 30 ns;

```

```
salidaCont <= "0101";
wait for 30 ns;
salidaCont <= "0110";
wait;
end process;
```

end Behavioral;

Código Mux:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity TB_Mux is
-- Port ( );
end TB_Mux;


architecture Behavioral of TB_Mux is
component mux is
Port ( salidaDeco : in STD_LOGIC_VECTOR (6 downto 0);
      op : in STD_LOGIC;
      salidaMux : out STD_LOGIC_VECTOR (6 downto 0));
end component;
SIGNAL salidaDeco : STD_LOGIC_VECTOR (6 downto 0) := "0000000";
SIGNAL op : STD_LOGIC := '0';
SIGNAL salidaMux : STD_LOGIC_VECTOR (6 downto 0) := "0000000";
begin
u5 : mux
Port map(
    salidaDeco => salidaDeco,
    op => op,
    salidaMux => salidaMux
);

stimulus: process
begin


op <= '0';
wait for 70 ns;
salidaDeco <= "0010101";
op <= '1';
wait for 70 ns;
salidaDeco <= "1111110";
op <= '0';
wait for 30 ns;
op <= '1';
wait;
end process;
end Behavioral;
```

Diagramas RTL:


RTL Completa:

 


RTL divisor:

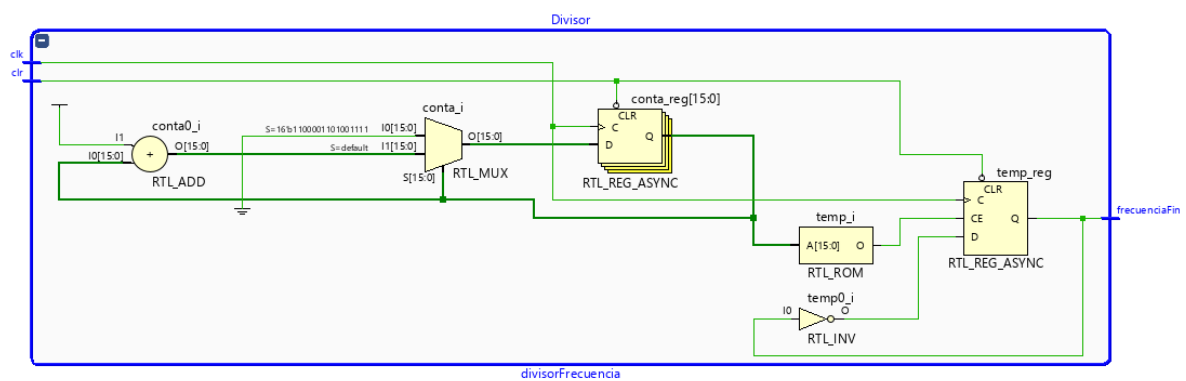


RTL UC:

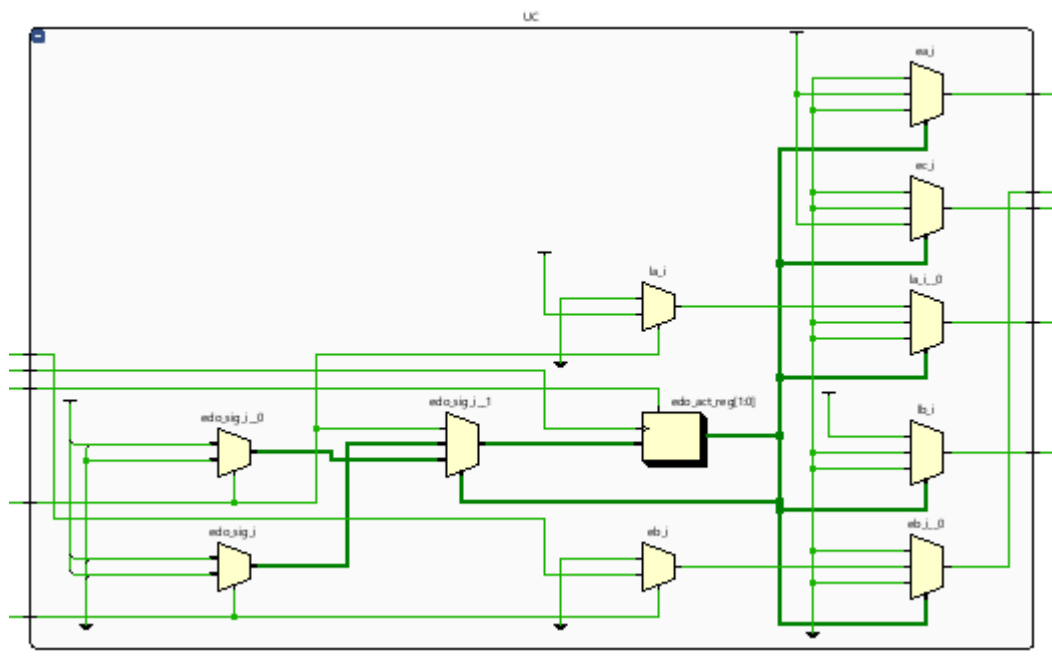


RTL Contador:

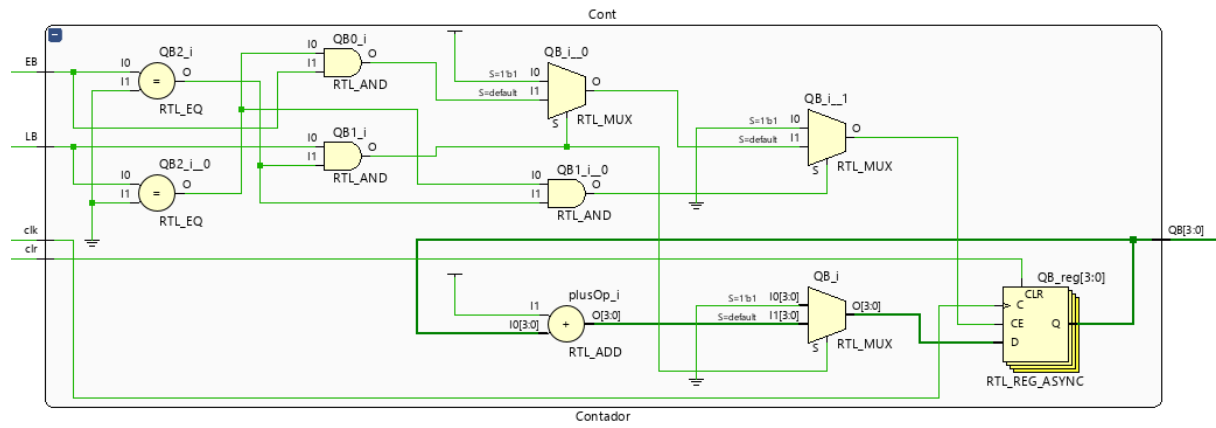


RTL Arreglo:

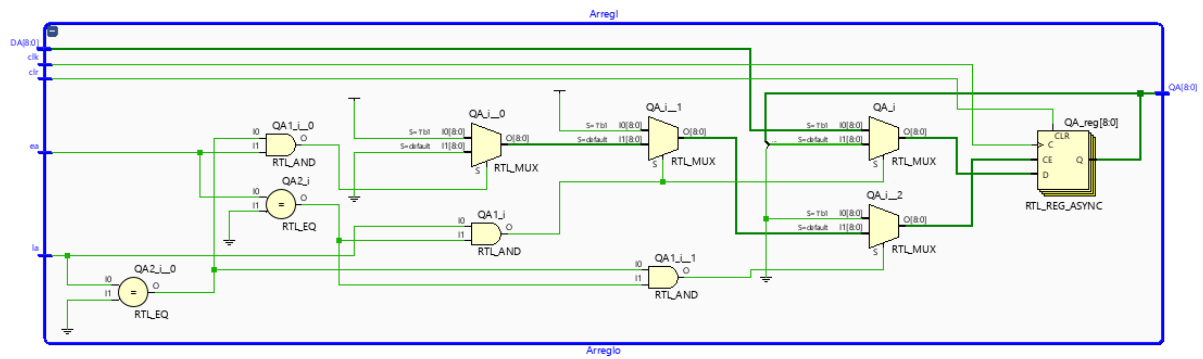

RTL Mux:

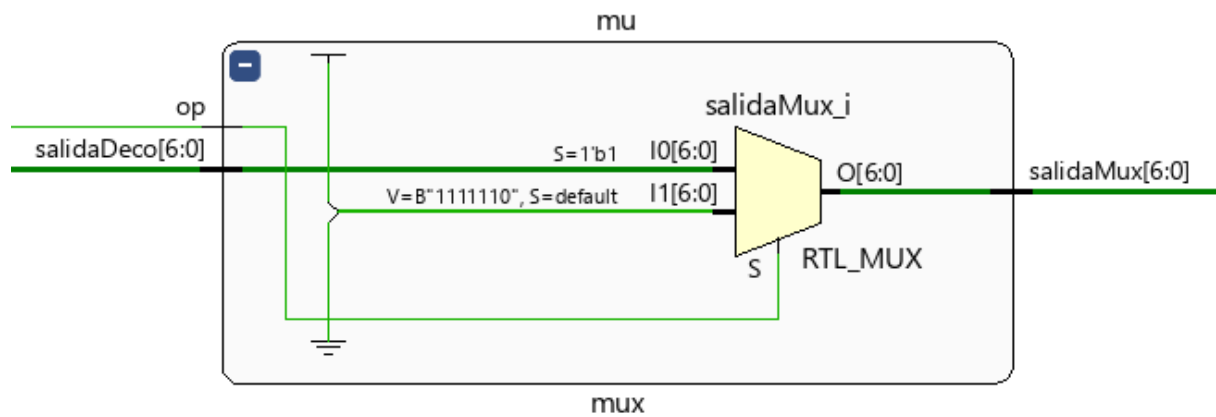


RTL Decodificador:

 


Simulaciones:


Simulación Completa:

 


Simulación Contador:

 


Simulación Arreglo:

 

Simulación Decodificador:

 

Simulación Mux:

 

Simulación UCS:

